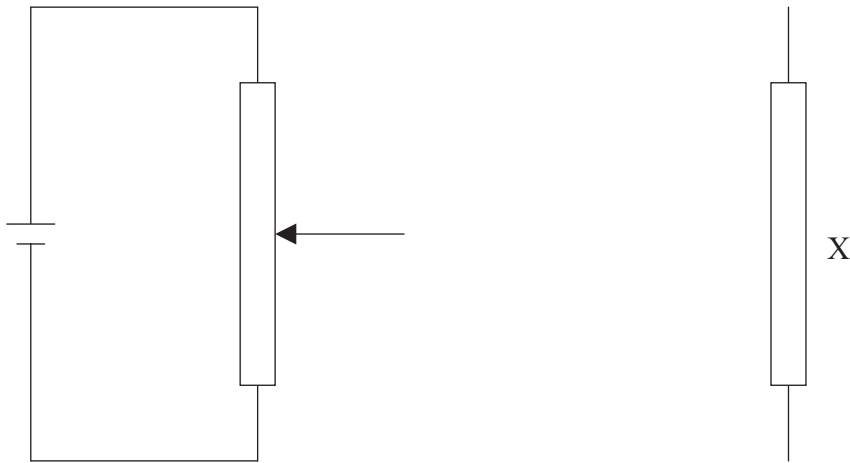



- A3.** (a) Draw the complete diagram of the circuit that uses a potential divider, ammeter, voltmeter and cell to measure the current-voltage characteristics for component X. [3]



(This question continues on the following page)

(Question A3 continued)

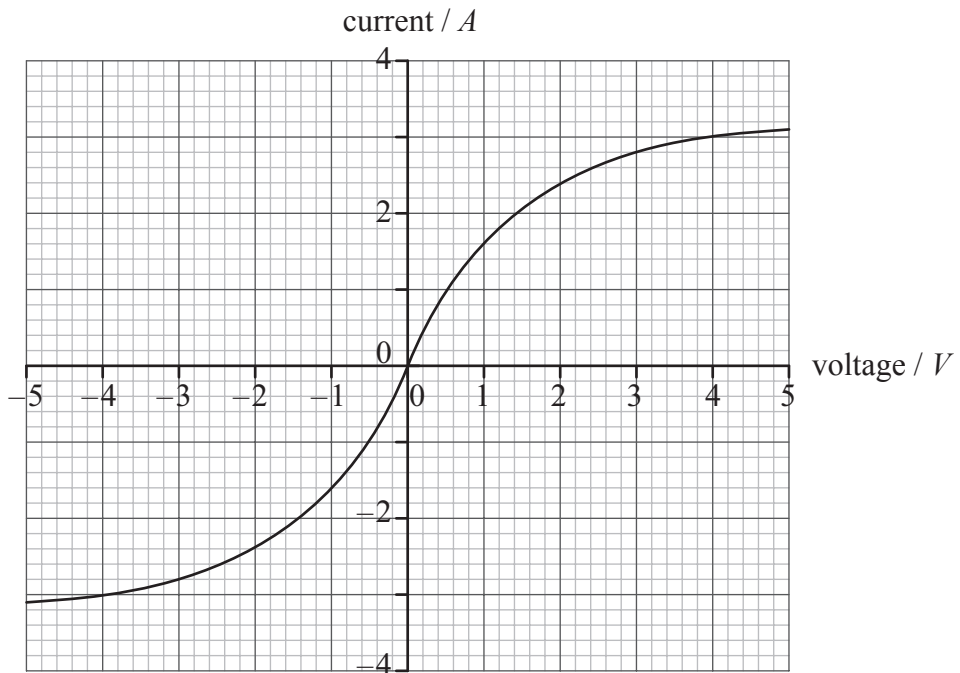- (b) The graph shows the current-voltage characteristics for the component X.



Component X is now connected across the terminals of a cell of emf 2.0 V and negligible internal resistance. Use the graph to show that the resistance of X is 0.83Ω . [2]

.....

.....

.....

.....

- (c) A resistor of constant resistance 1.0Ω is connected in series with the cell in (b) and with X. Use the graph to deduce that the current in the circuit is 1.3 A. [3]

.....

.....

.....

.....

.....



(Question B2 continued)

Part 2 Electrical resistance and electric circuits

- (a) Define *resistance* and state Ohm’s law. [2]

Resistance:

.....

Ohm’s law:

.....

- (b) A resistor made from a metal oxide has a resistance of $1.5\ \Omega$. The resistor is in the form of a cylinder of length 2.2×10^{-2} m and radius 1.2×10^{-3} m. Calculate the resistivity of the metal oxide. [2]

.....

.....

.....

.....

- (c) The manufacturer of the resistor in (b) guarantees its resistance to be within $\pm 10\%$ of $1.5\ \Omega$ provided the power dissipation in the resistor does not exceed 1.0 W. Calculate the maximum current in the resistor for the power dissipation to be equal to 1.0 W. [2]

.....


.....

(This question continues on the following page)



(Question B2, part 2 continued)

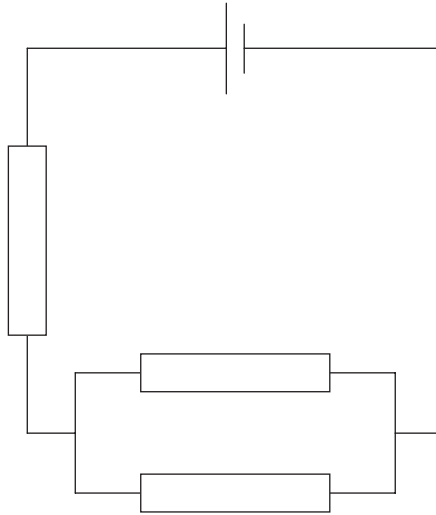- (d) The resistance of each of the resistors in the circuit below is measured to be $1.5\ \Omega$ with an accuracy of $\pm 10\%$.



The cell has an emf of 2.0 V and negligible internal resistance.

- (i) Define *emf*. [1]

.....

.....

- (ii) Determine the minimum and the maximum power that could be dissipated in this circuit. [3]

.....

.....

.....


.....

.....

B3. This question is in **two** parts. **Part 1** is about an electrical heater. **Part 2** is about heating a liquid.

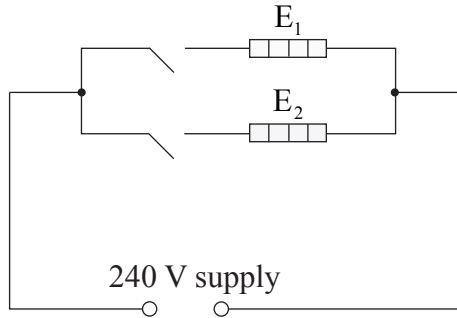Part 1 Electrical heater

An electrical heater consists of two heating elements E_1 and E_2 . The elements are connected in parallel. Each element has a switch and is connected to a supply of emf 240 V. The supply has negligible internal resistance.



Element E_1 is made from wire that has a cross-sectional area of $6.8 \times 10^{-8} \text{ m}^2$. The resistivity of the wire at the operating temperature of the element is $1.1 \times 10^{-6} \Omega \text{ m}$.

(a) (i) The total length of wire is 4.5 m. Show that the resistance of E_1 is 73Ω . [1]

.....

(ii) Calculate the power output of E_1 with only this element connected to the supply. [2]

.....

(iii) Element E_2 is made of wire of the same cross-section and material as E_1 . The length of wire used to make E_2 is 1.5 m. Determine the total power output when both E_1 and E_2 are connected to the supply. [3]

.....

(This question continues on the following page)



(Question B3, part 1 continued)

- (iv) With reference to the power output, explain why it would be inappropriate to connect the heating elements in series. [3]

.....

.....


.....

.....

.....


.....

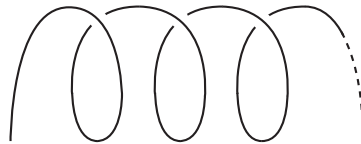- (b) Each element in the electrical heater is wound as a coil as shown.



Each turn of the coil may be considered to act as a current-carrying long straight wire.

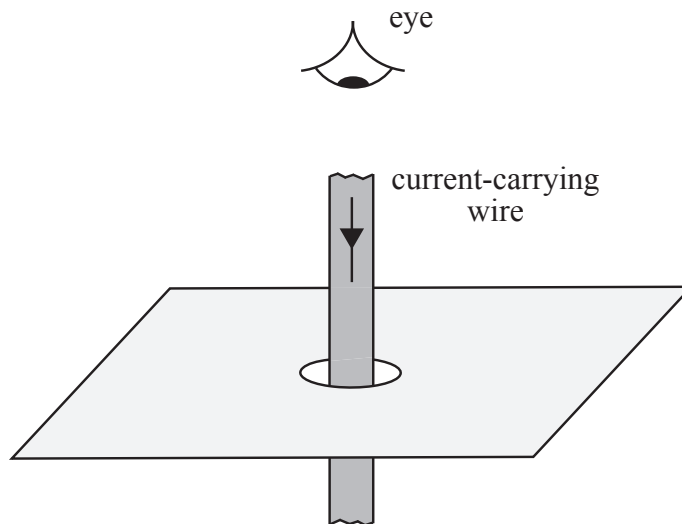- (i) On the diagram, draw the magnetic field around a current-carrying long straight wire. The arrow shows the direction of the current. [3]



- (ii) State **and** explain whether the turns of wire will attract or repel one another. [3]

.....

.....

.....

.....


.....

(This question continues on the following page)

(Question B2 continued)

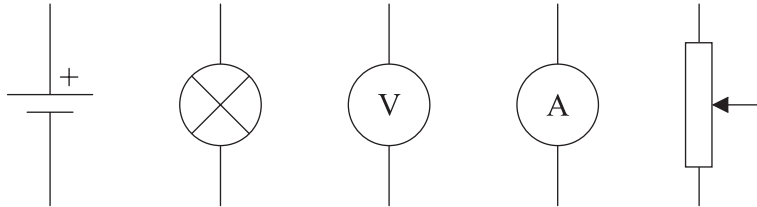Part 2 Electric circuits

The components shown below are to be connected in a circuit to investigate how the current I in a tungsten filament lamp varies with the potential difference V across it.




- (a) Construct a circuit diagram to show how these components should be connected together in order to obtain as large a range as possible for values of potential difference across the lamp. [4]

(This question continues on the following page)

(Question B2, part 2 continued)

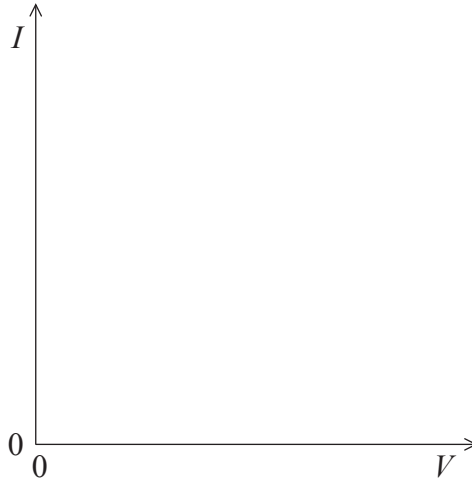- (b) On the axes, sketch a graph of I against V for a filament lamp in the range $V=0$ to its normal working voltage. [2]



- (c) The lamp is marked with the symbols “1.25 V, 300 mW”. Calculate the current in the filament when it is working normally. [1]

.....

- (d) The resistivity of tungsten at the lamp’s working temperature is $4 \times 10^{-7} \Omega \text{m}$. The total length of the tungsten filament is 0.80 m. Estimate the radius of the filament. [4]

.....

- (e) The cell is connected to two identical lamps connected in parallel. The lamps are rated at 1.25 V, 300 mW. The cell has an emf of 1.5 V and an internal resistance of 1.2Ω . Determine whether the lamps will light normally. [4]

.....



A2. This question is about electrical resistance.

(a) A heating coil is to be made of wire of diameter 3.5×10^{-4} m. The heater is to dissipate 980 W when connected to a 230 V d.c. supply. The material of the wire has resistivity $1.3 \times 10^{-6} \Omega \text{m}$ at the working temperature of the heater.

(i) Define *electrical resistance*. [1]

.....

(ii) Calculate the resistance of the heating coil at its normal working temperature. [2]

.....

(iii) Show that the length of wire needed to make the heating coil is approximately 4 m. [2]

.....

(This question continues on the following page)



