

B4. Part 1 Electrical heater

(a) (i) use of $R \left(= \frac{\rho l}{A} = \right) \frac{1.1 \times 10^{-6} \times 4.5}{6.8 \times 10^{-8}}$; [1]
72.8Ω (73Ω)

(ii) $\frac{240^2}{72.8}$ / shows appropriate alternative equation;
790 W; [2]

(iii) one-third length so E_2 has one-third resistance of E_1 / evaluates R (24Ω);
(same V so) $3 \times$ power of E_1 ;
so total power = $4 \times E_1 = 3.2$ kW; [3]

or numerical method

$$\text{current in } R_1 = \frac{728}{240} = 3 \text{ A};$$

$$\text{current in } R_2 = 9 \text{ A};$$

$$\text{total current} = 12 \text{ A and total power} = 3.2 \text{ kW};$$

Award [3] for correct alternative working.

(iv) the power output will be less;
because the total resistance is greater in the series case;
hence the current is less and power depends on I^2 ;

$$P = \frac{V^2}{R};$$

[3 max]

SECTION B**B1. Part 1** Electrical fields and electrical resistance

(a) a conductor contains “free” electrons and insulators do not / *OWTTE*; [1]

(b) to have a current electrons must be accelerated/move along the wire;
and so a (electric) force must act on them;
this is provided by the electric field; [3]

(c) 8.8×10^{-18} N; [1]

(d) the ratio of potential difference across a device/load/resistor to current in the device/load/resistor; [1]

(e) $\rho = \frac{RA}{l}$;
 $= \left(\frac{1.5 \times \pi \times 1.2^2 \times 10^{-6}}{2.2 \times 10^{-2}} \right) 3.1 \times 10^{-4} \Omega \text{m};$ [2]

(f) $I = \left(\sqrt{\frac{P}{R}} = \right) \sqrt{\frac{1}{1.35}}$;
 $= 0.86 \text{ A};$ [2]

(g) (i) the power supplied per unit current / work done per unit charge in moving charge completely round the circuit / energy per unit charge made available by the source; [1]

(ii) minimum resistance is 2.0Ω , maximum resistance is 2.5Ω ;


so maximum power is $\left(\frac{2.0^2}{2.0} \right) = 2.0 \text{ W};$

and minimum power is $\left(\frac{2.0^2}{2.5} \right) = 1.6 \text{ W};$ [3]

B4. Part 1 Electric circuits


- (a) any circuit in which the current will flow through the lamp;
 variable resistor connected as a potential divider;
 voltmeter across lamp;
 ammeter in series with lamp;

[4]

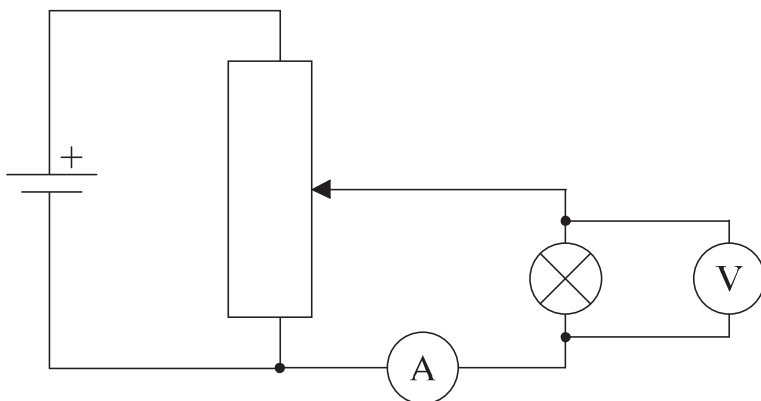

- (b) correct shape;
 through origin;

[2]

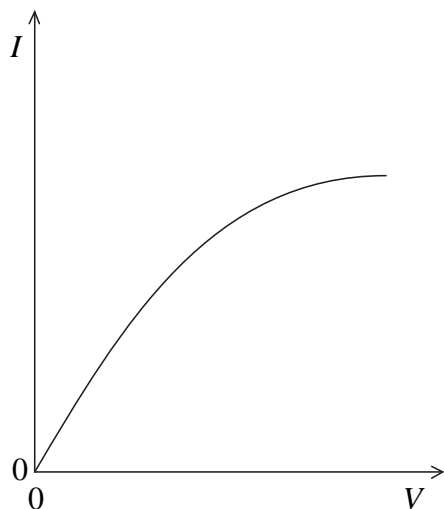

- (c) 0.24 A;

[1]

- (d) resistance calculated = 5.2(Ω);

$$A = \left(\frac{\rho l}{R} \right) = 6.2 \times 10^{-8} \text{ m}^2 ;$$

$$\text{radius} = \sqrt{\frac{A}{\pi}} \text{ seen/used;}$$

$$= 1.4 \times 10^{-4} \text{ m ;}$$

[4]

(e) calculates resistance of lamps in parallel ($2.6\ \Omega$);

$V = \mathcal{E} - Ir$ used to give $V = 1.0\ \text{V}$;

$1.0\ \text{V}$ is lower than $1.25\ \text{V}$ / power available to each lamp is $192\ \text{mW}$ lower than $300\ \text{mW}$;

(terminal pd/power lower) hence not operating normally; $\left\{ \begin{array}{l} \text{Award [0] for only stating} \\ \text{this bald answer.} \end{array} \right.$

[4]

Watch for ECF from (d).

Award [4 max] for any correct numerical argument involving energy or power calculations.


SECTION A

- A1.** (a) (i) no
the graph is not linear / not a straight line; [1]
- (ii) a straight horizontal line through the initial points along the T axis;
a smooth curve through the remaining points ($T = 4.4$ to 7.0 K); [2]
The straight line and curve do not need to be joined.
- (b) $R = 0\Omega$; [1]
Do not apply unit mark.
- (c) (i) $4.2 - 4.4$ K; [1]
- (ii) 4.3 K; [2]
 ± 0.1 (K);
allow ECF from (c)(i)
- (iii) more sensitive thermometer / thermometer with a finer graduated scale /
by taking resistance measurements at smaller temperature intervals; [1]
Award [0] for electronic digital thermometer only.
- (d) the data are for low temperatures well below room temperature;
no reason to assume the trend will continue to room temperature;
the data shows R varying sharply at T_C and another such transition might take place
below room temperature;
mercury is a liquid at room temperature; [2 max]
Award any other sensible answer.

SECTION B

B1. Part 1 ~~Electric fields and electric circuits~~

(a) (i)

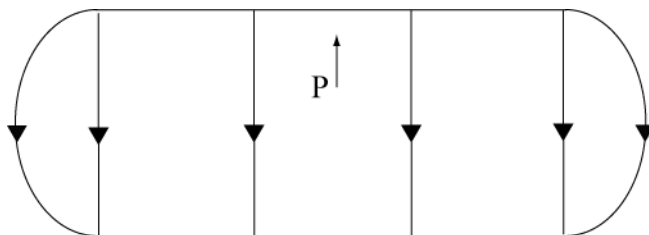

~~uniform field equal spacing of lines;
edge effect;
direction;~~

[3]

(ii) as shown;

[1]

(b) ~~combine $F = qE$ and $F = ma$;~~

~~to get $E = \frac{ma}{q}$;~~

~~$E = 5.0 \times 10^3 \text{ N C}^{-1} / \text{V m}^{-1}$;~~

[3]

(c) ~~$V = \frac{1.9 \times 10^{-17}}{1.6 \times 10^{-19}}$;~~
 ~~$= 120 \text{ V}$~~

[1]

(d) (i) 3.0 W;

[1]

(ii) power dissipated in battery $= (0.25^2 \times 4.0) = 0.25 \text{ W}$;power dissipated in circuit $= (3.0 - 0.25) = 2.8 (2.75) \text{ W}$;

[2]

(iii) power dissipated in lamp $= (3.0 \times 0.25) = 0.75 \text{ W}$;power dissipated in resistor $= (2.75 - 0.75) = 2.0 \text{ W}$;resistance $\left(= \frac{2.0}{0.25^2} \right) = 32 \Omega$;


[3]

*or*resistance of lamp $= 12 \Omega$; $12 = 0.25(R + 16)$; $R = 32 \Omega$;*or* V across $R = 8.0 \text{ V}$; $R = \frac{8.0}{0.25}$; $= 32 \Omega$;

A2. (a) (i) ratio of potential difference to current / $\frac{V}{I}$ with terms defined; [1]

(ii) resistance = $\frac{230^2}{980}$;
 = 54Ω ; [2]
Award [2] for bald correct answer.

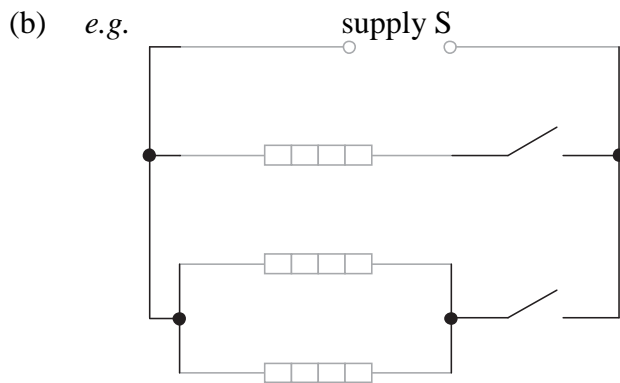(iii) $L = \frac{RA}{\rho}$;
 $= \frac{54 \times \pi \times [1.75 \times 10^{-4}]^2}{1.3 \times 10^{-6}}$;
 ($L \approx 4\text{ m}$) [2]
Must see re-arrangement of data booklet equation or completely correct substitution as shown in second line for first mark.



switch connected so that P can be achieved;
 another switch connected so that $2P$ and $3P$ can be achieved; [2]
Award [0] if three or more switches used. Allow any correct alternative including case where single resistor is permanently connected to supply. There are many variants, this diagram is only one example.

A3. (a) region/area/volume (of space);
 where a mass/charge experiences a force; [2]

(b)

Particle	Charge on particle	Initial direction of motion of particle	Direction of force on particle	Type of field
A	uncharged	stationary	in direction of field	gravitational;
B	negative	along direction of field	opposite to direction of field	electric; (accept electrostatic)
C	positive	normal to direction of field	normal to direction of field	magnetic;

[3]

B4. Part 1 Domestic shower

(a) (i) the amount of energy/heat required to raise the temperature of 1kg of a substance through 1K / 1°C; [1]

(ii) energy supplied by heater in 1s = 7.2×10^3 J ;
 energy per second = mass per second \times sp ht \times rise in temperature;
 $7.2 \times 10^3 = \text{mass per second} \times 4.2 \times 10^3 \times 26$;
 to give mass per second = 0.066kg ; [4]

(iii) energy is lost to the surroundings;
 flow rate is not uniform; [2]
Do not allow "the heating element is not in contact with all the water flowing in the unit".

(iv) $P = VI$ $I = \frac{P}{V}$;
 $= \frac{7.2 \times 10^3}{240} = 30$ A ; [2]

(v) when operating at 7.2 kW the element is at a higher temperature/hotter than when first switched on;
 therefore, resistance is greater (and so current is smaller) / *OWTTE*;
or
 element is cold /*OWTTE* when first switched on;
 therefore, smaller resistance than when hot (and so current is larger); [2]

(b) $P = \frac{V^2}{R}$;
 $\frac{240^2}{R_{240}} = \frac{110^2}{R_{110}}$;
 $\frac{R_{110}}{R_{240}} = \left(\frac{110}{240} \right)^2$;
 = 0.21

or

from $P = VI$

$240I_2 = 110I_1$ to give $I_2 = \frac{11}{24} I_1$;

$I_2^2 R_2 = I_1^2 R_1$;

$\frac{R_1}{R_2} = \frac{I_2^2}{I_1^2} = \left(\frac{11}{24} \right)^2$;
 = 0.21

[3 max]