

~~A2. (a)  $11 \text{ ms}^{-2}$ ; [1]~~

~~(b)  $\Delta v = 236$ ;  
 $a = \left( \frac{236}{8} \right) = 29.5 \text{ (ms}^{-2}\text{)}$ ;  
 $(F = 1.1 \times 10^4 \times 29.5) = 3.2 \times 10^5 \text{ N}$ ; [3]~~


~~Award [2 max] for omission of initial speed (answer is 390 kN).~~

~~(c) phase 1 distance 88 m / phase 2 distance 1296 m;  
 total 1400 m; [2]  
 Watch for significant figure penalty in this question (1384 m).~~

~~Award [1 max] for  $\frac{1}{2}at^2$  substituted correctly for first phase, if no distances evaluated and answer incorrect.~~

~~Award [1 max] for correct addition of incorrect phase 1 and/or 2 distance(s).~~

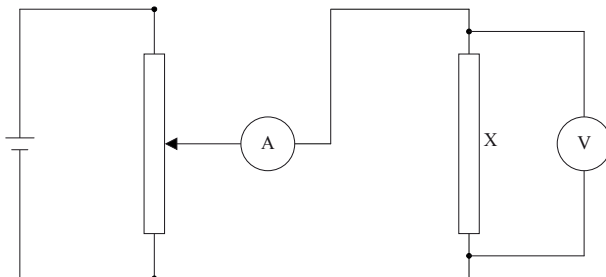A3. (a) voltmeter in parallel across X;  
 ammeter in series with X;  
 correct circuit; (allow ecf from 1st and 2nd marking points) [3]  
 Accept voltmeter connections that include ammeter (in series with X)  
 Condone re-drawing of resistor X closer to variable resistor.



(b)  $I = 2.4 \text{ A}$  at  $2.0 \text{ V}$ ;  
 $\frac{2}{2.4}$ ;  
 $= 0.83 \Omega$  [2]

Award [1 max] for use of gradient of graph from (2,2.4) to origin.

(c) total p.d. across  $1 \Omega$  resistor =  $1.3 \text{ (V)}$ ;  
 p.d. across X =  $0.7 \text{ (V)}$ ;  
 reading from graph  $I = 1.3 \text{ A}$  at  $0.7 \text{ V}$  / evidence that the graph has been read; [3]  
 Award [1 max] if value of calculated p.d. is incorrect but there is clear graphical evidence of derivation of current (typically marks on graph).

or

total p.d. across X + resistor =  $2.0 \text{ (V)}$ ;  
 this occurs when  $V_X = 0.7 \text{ (V)}$  and  $V_{1.0} = 1.3 \text{ (V)}$ ;  
 at  $I = 1.3 \text{ A}$ ;

**Part 2** Electrical resistance and electric circuits

- (a) *resistance*: the ratio of potential difference across a device/load/resistor to current in the device/load/resistor;

*Ohm's law*: the resistance of a conductor is constant provided its temperature is constant / the current is proportional to the voltage across; [2]

(b)  $\rho = \frac{RA}{l}$ ;  
 $= \left( \frac{1.5 \times \pi \times 1.2^2 \times 10^{-6}}{2.2 \times 10^{-2}} \right) = 3.1 \times 10^{-4} \Omega \text{m}$ ; [2]

(c)  $I = \left( \sqrt{\frac{P}{R}} = \right) \sqrt{\frac{1}{1.35}}$ ;  
 $= 0.86 \text{A}$ ; [2]

- (d) (i) the power supplied per unit current / work done per unit charge in moving charge completely round the circuit / energy per unit charge made available by the source; [1]

(ii) minimum resistance is  $2.0 \Omega$ , maximum resistance is  $2.5 \Omega$ ;

so maximum power is  $\left( \frac{2.0^2}{2.0} \right) = 2.0 \text{W}$ ;

and minimum power is  $\left( \frac{2.0^2}{2.5} \right) = 1.6 \text{W}$ ; [3]

**B3. Part 1** Electrical heater

(a) (i) use of  $R \left( = \frac{\rho l}{A} = \right) \frac{1.1 \times 10^{-6} \times 4.5}{6.8 \times 10^{-8}}$ ; [1]  
 72.8Ω (73Ω)

(ii)  $\frac{240^2}{72.8}$  / shows appropriate alternative equation;  
 790 W; [2]

(iii) one-third length so  $E_2$  has one-third resistance of  $E_1$  / evaluates  $R$  (24Ω);  
 (same V so)  $3 \times$  power of  $E_1$ ;  
 so total power =  $4 \times E_1 = 3.2$  kW; [3]

*or numerical method*

current in  $R_1 = \frac{728}{240} = 3$  A;

current in  $R_2 = 9$  A;

total current = 12 A and total power = 3.2 kW;

*Award [3] for correct alternative working.*

(iv) the power output will be less;  
 because the total resistance is greater in the series case;  
 hence the current is less and power depends on  $I^2$ ;


$P = \frac{V^2}{R}$ ;

[3 max]

**Part 2** Electric circuits


- (a) any circuit in which the current will flow through the lamp;  
 variable resistor connected as a potential divider;  
 voltmeter across lamp;  
 ammeter in series with lamp;

[4]

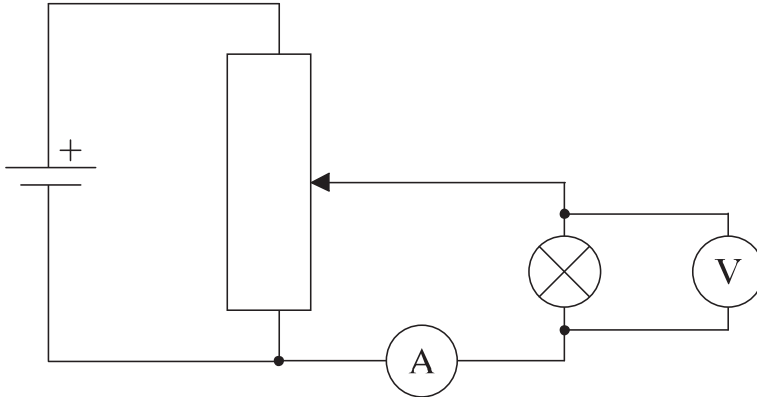

- (b) correct shape;  
 through origin;

[2]

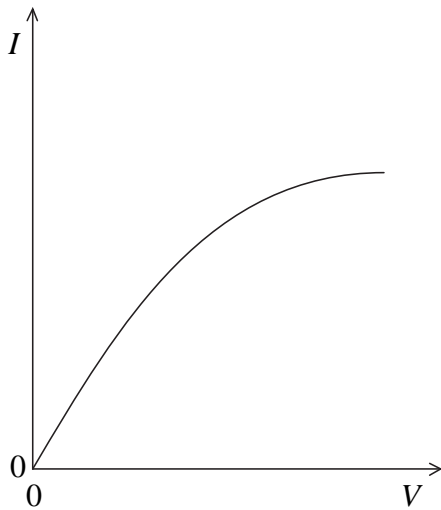

- (c) 0.24 A;

[1]

- (d) resistance calculated = 5.2 ( $\Omega$ );

$$A = \left( \frac{\rho l}{R} \right) = 6.2 \times 10^{-8} \text{ m}^2 ;$$

$$\text{radius} = \sqrt{\frac{A}{\pi}} \text{ seen/used;}$$

$$= 1.4 \times 10^{-4} \text{ m ;}$$

[4]

(e) calculates resistance of lamps in parallel ( $2.6\ \Omega$ );

$V = \mathcal{E} - Ir$  used to give  $V = 1.0\ \text{V}$ ;

$1.0\ \text{V}$  is lower than  $1.25\ \text{V}$  / power available to each lamp is  $192\ \text{mW}$  lower than  $300\ \text{mW}$ ;

(terminal pd/power lower) hence not operating normally;  $\left\{ \begin{array}{l} \text{Award [0] for only stating} \\ \text{this bald answer.} \end{array} \right.$

[4]

*Watch for ECF from (d).*

*Award [4 max] for any correct numerical argument involving energy or power calculations.*

A2. (a) (i) ratio of potential difference to current /  $\frac{V}{I}$  with terms defined; [1]


(ii) resistance =  $\frac{230^2}{980}$ ;  
 =  $54\Omega$ ; [2]

*Award [2] for bald correct answer.*

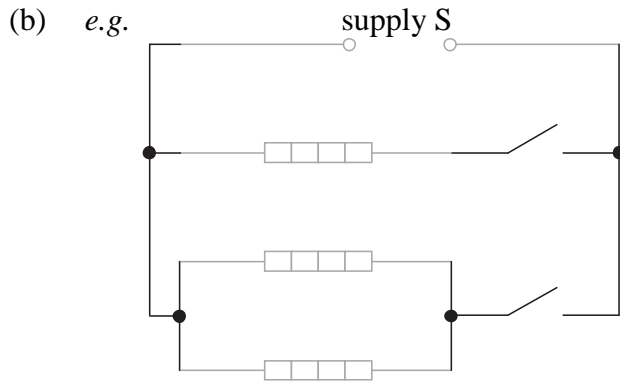(iii)  $L = \frac{RA}{\rho}$ ;  
 $= \frac{54 \times \pi \times [1.75 \times 10^{-4}]^2}{1.3 \times 10^{-6}}$ ;

( $L \approx 4\text{m}$ ) [2]


*Must see re-arrangement of data booklet equation or completely correct substitution as shown in second line for first mark.*



switch connected so that  $P$  can be achieved;  
 another switch connected so that  $2P$  and  $3P$  can be achieved; [2]  
*Award [0] if three or more switches used. Allow any correct alternative including case where single resistor is permanently connected to supply. There are many variants, this diagram is only one example.*

**Part 2** Electric fields and electric circuits

(a) (i)

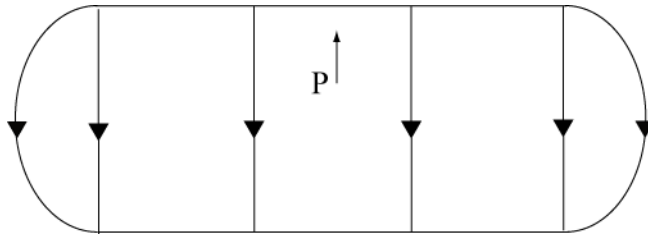

uniform field equal spacing of lines;  
edge effect;  
direction;

[3]

(ii) as shown;

[1]

(b) combine  $F = qE$  and  $F = ma$ ;

to get  $E = \frac{ma}{q}$ ;

$E = 5.0 \times 10^3 \text{ N C}^{-1} / \text{V m}^{-1}$ ;

[3]

(c)  $V = \frac{1.9 \times 10^{-17}}{1.6 \times 10^{-19}}$ ;  
 $= 120 \text{ V}$

[1]

(d) (i) 3.0 W;

[1]

(ii) power dissipated in battery  $= (0.25^2 \times 4.0) = 0.25 \text{ W}$ ;

power dissipated in circuit  $= (3.0 - 0.25) = 2.8 (2.75) \text{ W}$ ;

[2]

(iii) power dissipated in lamp  $= (3.0 \times 0.25) = 0.75 \text{ W}$ ;

power dissipated in resistor  $= (2.75 - 0.75) = 2.0 \text{ W}$ ;

resistance  $\left( = \frac{2.0}{0.25^2} \right) = 32 \Omega$ ;

[3]

*or*

resistance of lamp  $= 12 \Omega$ ;

$12 = 0.25 (R + 16)$ ;

$R = 32 \Omega$ ;

*or*

V across  $R = 8.0 \text{ V}$ ;

$R = \frac{8.0}{0.25}$ ;

$= 32 \Omega$ ;

[3]

- A2. (a) there are no positions;  
the lamp is effectively in series with  $100\text{k}\Omega$  no matter what the position of S;  
this means that the pd across it will always be close to zero (very small) / never reach  $6\text{V}$ ;

or

the resistance of the filament is much smaller than  $100\text{k}\Omega$  ;

so (nearly) all the potential of the battery appears across the variable resistance;


Award [0] for incorrect argument or just the answer without any explanation.

[3]

(b) 
$$I = \frac{V}{R};$$

$$= \frac{12}{10^5} = 1.2 \times 10^{-4} \text{ A};$$

[2]

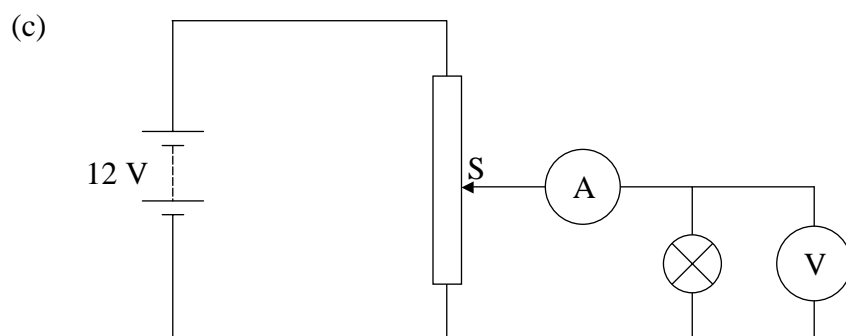

correct position of ammeter;

correct position of voltmeter (either to the right or left of the lamp);

[2]

- ~~A3. (a) the force exerted per unit mass;  
on a point (small) mass;~~

~~[2]~~

(b) (i) ~~use of  $g = \frac{F}{m}$  and  $F = G \frac{Mm}{R^2}$  ;~~  
~~combine to get  $g = G \frac{M}{R^2}$  ;~~

~~[2]~~

(ii)  ~~$M = \frac{gR^2}{G}$  ;~~

~~substitute to get  $M = 1.9 \times 10^{27} \text{ kg}$  ;~~

~~[2]~~