

Voltage and Current in Circuits

For each of the circuits shown here, find the current and voltage at each bulb and power supply.

