

Solving Complete VIR Circuits

1. Calculate:

a) the total current in the circuit.

$$R_T = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} + R_3$$

$$R_T = \left(\frac{1}{40\ \Omega} + \frac{1}{60\ \Omega} \right)^{-1} + 16\ \Omega$$


$$R_T = 40\ \Omega$$

$$V = IR$$

$$I = \frac{V}{R} = \frac{10\text{ V}}{40\ \Omega} = 0.25\text{ A}$$

b) the current in the 60 Ω resistor.

$$I = 0.1\text{ A}$$

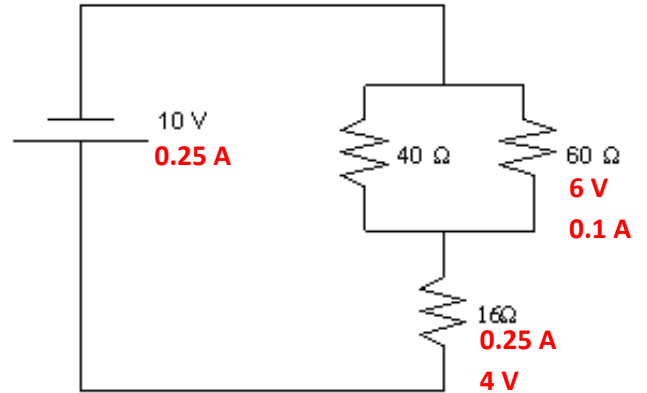

2. Calculate:

a) the total resistance.

$$R_T = R_1 + \left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

$$R_T = 4\ \Omega + \left(\frac{1}{10\ \Omega} + \frac{1}{15\ \Omega} \right)^{-1}$$

$$R_T = 10\ \Omega$$


b) the total current.

$$V = IR$$

$$I = \frac{V}{R} = \frac{10\text{ V}}{10\ \Omega} = 1\text{ A}$$

c) the current through the 15 Ω resistor

$$I = 0.4\text{ A}$$

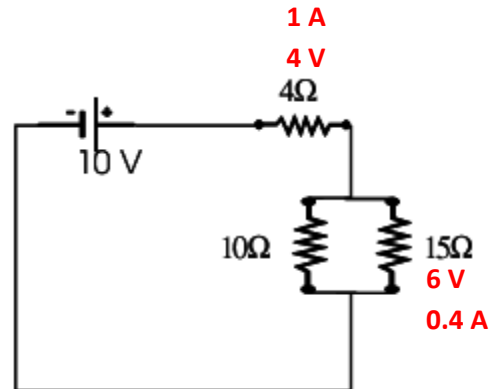

3. Calculate.

a) the total resistance.

$$R_T = \left(\frac{1}{R_1+R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)^{-1}$$

$$R_T = \left(\frac{1}{3\ \Omega} + \frac{1}{3\ \Omega} + \frac{1}{4\ \Omega} \right)^{-1}$$

$$R_T = 1.09\ \Omega$$

b) the total current.

$$V = IR$$


$$I = \frac{V}{R} = \frac{5\text{ V}}{1.09\ \Omega} = 4.6\text{ A}$$

c) the current through the 4 Ω resistor.

$$I = 1.25\text{ A}$$

d) voltage across the 2 Ω resistor.

$$V = 3.3\text{ V}$$

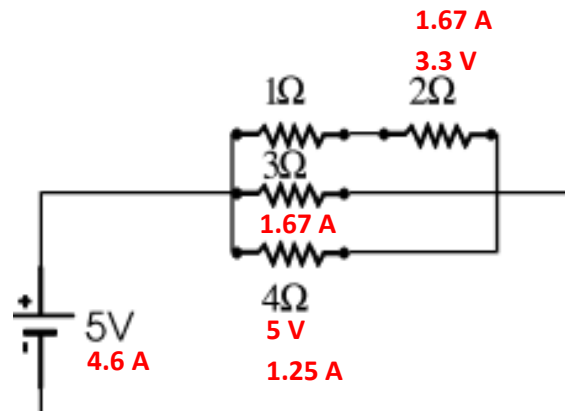

4. Calculate:

a) the total resistance.

$$R_T = \left(\frac{1}{R_1+R_2} + \frac{1}{R_3+R_4} \right)^{-1}$$

$$R_T = \left(\frac{1}{3\Omega+3\Omega} + \frac{1}{4\Omega+2\Omega} \right)^{-1}$$

$$R_T = 3\Omega$$


b) the total current.

$$V = IR$$

$$I = \frac{V}{R} = \frac{6V}{3\Omega} = 2A$$

c) the current through the 4 Ω resistor

$$I = 1A$$

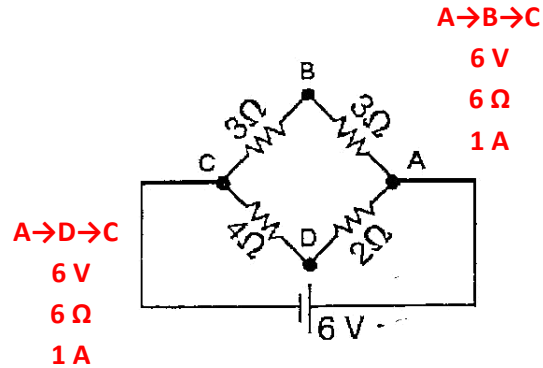

5. Calculate:

a) the total resistance.

$$R_T = R_1 + \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)^{-1} + R_5$$

$$R_T = 1\Omega + \left(\frac{1}{3\Omega} + \frac{1}{4\Omega} + \frac{1}{5\Omega} \right)^{-1} + 2\Omega$$

$$R_T = 4.28\Omega$$

b) the total current.

$$V = IR$$


$$I = \frac{V}{R} = \frac{12V}{4.28\Omega} = 2.81A$$

c) the current through the 4 Ω resistor.

$$I = 0.89A$$

d) voltage across the 2 Ω resistor.

$$V = 5.62V$$

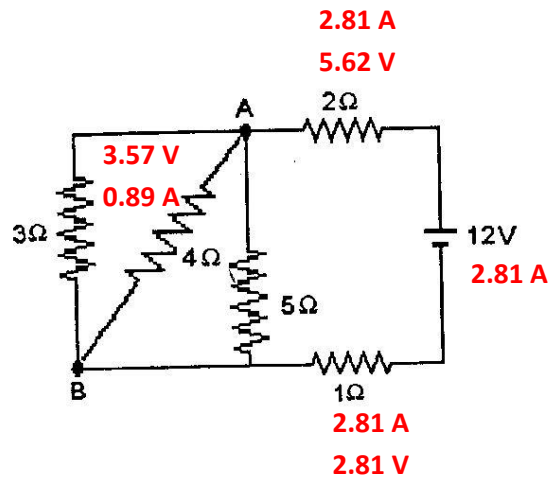

6. Calculate:

a) the total resistance.

$$R_T = R_1 + \left(\frac{1}{R_2+R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right)^{-1} + R_6$$

$$R_T = 6\Omega + \left(\frac{1}{15\Omega + 5\Omega} + \frac{1}{60\Omega} + \frac{1}{30\Omega} \right)^{-1} + 14\Omega$$

$$R_T = 30\Omega$$

b) the total current.

$$V = IR$$


$$I = \frac{V}{R} = \frac{15V}{30\Omega} = 0.5A$$

c) the current through the 30 Ω resistor.

$$I = 0.17A$$

d) the voltage across the 5 Ω resistor.

$$V = 1.25V$$

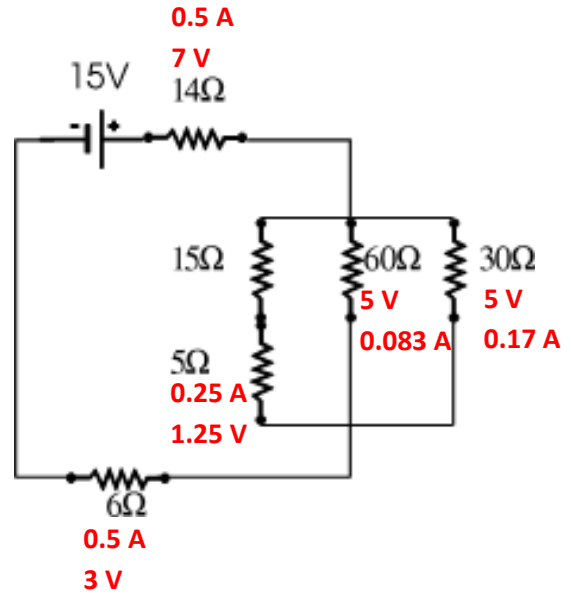


7. Calculate the value of the unknown resistor.

$$R_T = \left(\frac{1}{R_1+R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)^{-1}$$


$$R_T = \left(\frac{1}{7\Omega + 15\Omega} + \frac{1}{44\Omega} + \frac{1}{66\Omega} \right)^{-1}$$

$$R_T = 12\Omega$$

$$R = 9.3\Omega$$

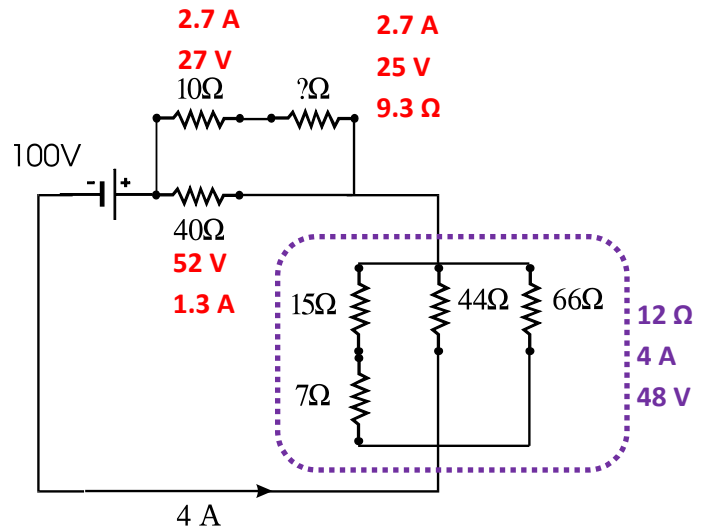

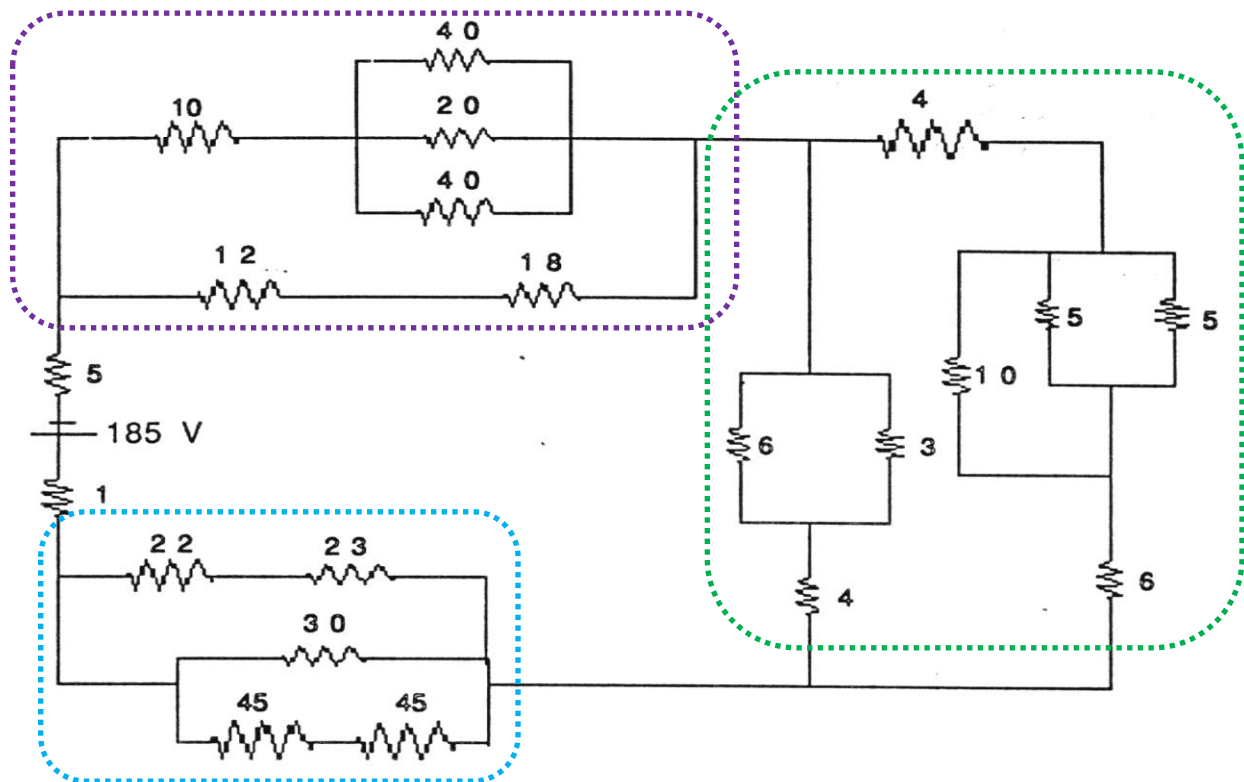8. Solve for the current travelling through the power supply in the circuit shown.



$$R_T = \left(\frac{1}{R_1 + \left(\frac{1}{R_2 + \frac{1}{R_3 + R_4}} \right)^{-1}} + \frac{1}{R_5 + R_6} \right)^{-1}$$

$$R_T = \left(\frac{1}{10\Omega + \left(\frac{1}{40\Omega + \frac{1}{20\Omega + 40\Omega}} \right)^{-1}} + \frac{1}{12\Omega + 18\Omega} \right)^{-1}$$

$$R_T = 12\Omega$$

$$R_T = \left(\frac{1}{R_1 + R_2} + \frac{1}{R_3} + \frac{1}{R_4 + R_5} \right)^{-1}$$

$$R_T = \left(\frac{1}{22\Omega + 23\Omega} + \frac{1}{30\Omega} + \frac{1}{45\Omega + 45\Omega} \right)^{-1}$$

$$R_T = 15\Omega$$

$$R_T = R_1 + R_T + R_T + R_T + R_2$$

$$R_T = 5\Omega + 12\Omega + 4\Omega + 15\Omega + 1\Omega$$

$$R_T = 37\Omega$$

$$V = IR$$

$$I = \frac{V}{R} = \frac{185V}{37\Omega} = 5A$$

$$R_T = \left(\frac{1}{R_1 + \left(\frac{1}{R_2 + \frac{1}{R_3 + R_4}} \right)^{-1} + R_5} + \frac{1}{\left(\frac{1}{R_6 + R_7} \right)^{-1} + R_8} \right)^{-1}$$

$$R_T = \left(\frac{1}{4\Omega + \left(\frac{1}{5\Omega + \frac{1}{5\Omega + 10\Omega}} \right)^{-1} + 6\Omega} + \frac{1}{\left(\frac{1}{6\Omega + 3\Omega} \right)^{-1} + 4\Omega} \right)^{-1}$$

$$R_T = 4\Omega$$